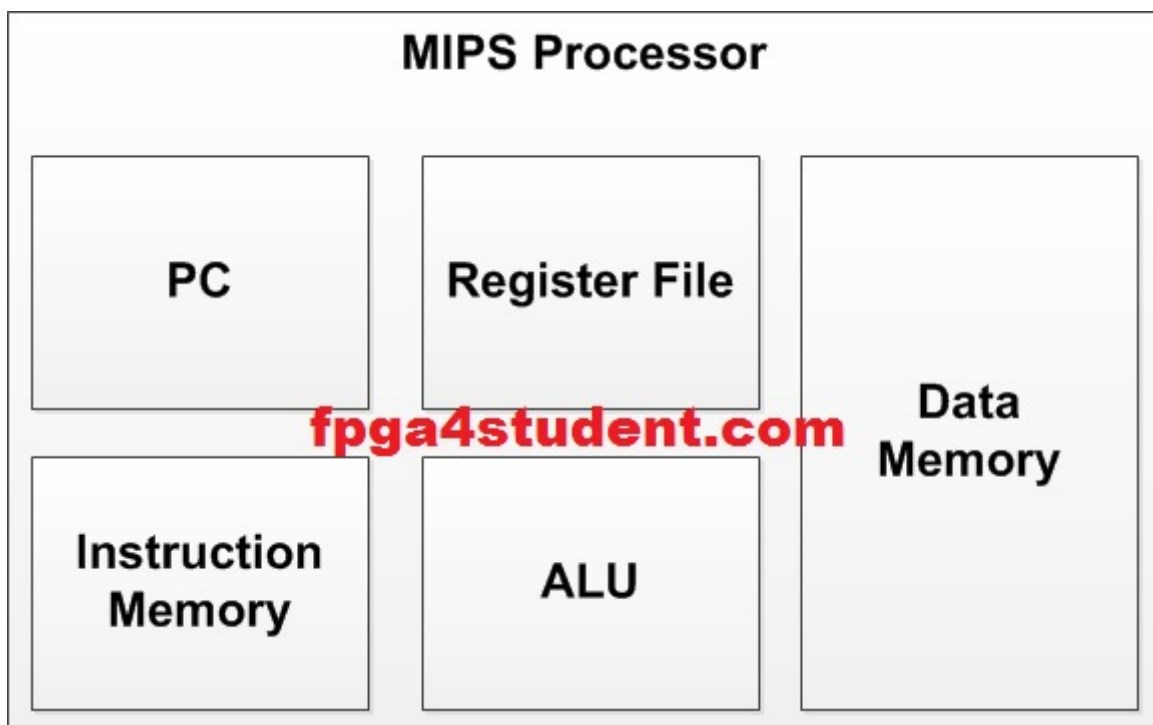


VHDL code for MIPS Processor

Last time, I presented a Verilog code for a 16-bit single-cycle MIPS processor. The instruction set and architecture design for the MIPS processor was provided [here](#).

Today, the **VHDL** code for the **MIPS Processor** will be presented. A simple **VHDL** testbench for the MIPS processor will be also provided for simulation purposes.



VHDL code for Data Memory of the MIPS processor:

```
-- fpga4student.com: FPGA projects, Verilog projects, VHDL projects
-- VHDL project: VHDL code for single-cycle MIPS Processor
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
USE IEEE.numeric_std.all;
-- VHDL code for the data Memory of the MIPS Processor
entity Data_Memory_VHDL is
port (
  clk: in std_logic;
  mem_access_addr: in std_logic_Vector(15 downto 0);
  mem_write_data: in std_logic_Vector(15 downto 0);
  mem_write_en, mem_read: in std_logic;
  mem_read_data: out std_logic_Vector(15 downto 0)
);
```

```

end Data_Memory_VHDL;

architecture Behavioral of Data_Memory_VHDL is
signal i: integer;
signal ram_addr: std_logic_vector(7 downto 0);
type data_mem is array (0 to 255) of std_logic_vector (15 downto 0);
signal RAM: data_mem :=((others=> (others=>'0')));
begin

    ram_addr <= mem_access_addr(8 downto 1);
    process(clk)
    begin
        if(rising_edge(clk)) then
            if (mem_write_en='1') then
                ram(to_integer(unsigned(ram_addr))) <= mem_write_data;
            end if;
        end if;
    end process;
    mem_read_data <= ram(to_integer(unsigned(ram_addr))) when (mem_read='1') else

end Behavioral;

```

VHDL code for ALU of the MIPS processor:

```

-- fpga4student.com: FPGA projects, Verilog projects, VHDL projects
-- VHDL project: VHDL code for single-cycle MIPS Processor
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_signed.all;
-- VHDL code for ALU of the MIPS Processor
entity ALU_VHDL is
port(
    a,b : in std_logic_vector(15 downto 0); -- src1, src2
    alu_control : in std_logic_vector(2 downto 0); -- function select
    alu_result: out std_logic_vector(15 downto 0); -- ALU Output Result
    zero: out std_logic -- Zero Flag
);
end ALU_VHDL;

architecture Behavioral of ALU_VHDL is
signal result: std_logic_vector(15 downto 0);
begin
    process(alu_control,a,b)
    begin
        case alu_control is
            when "000" =>
                result <= a + b; -- add
            when "001" =>
                result <= a - b; -- sub
            when "010" =>
                result <= a and b; -- and
            when "011" =>
                result <= a or b; -- or
            when "100" =>
                if (a<b) then

```

```

    result <= x"0001";
else
    result <= x"0000";
end if;
when others => result <= a + b; -- add
end case;
end process;
zero <= '1' when result=x"0000" else '0';
alu_result <= result;
end Behavioral;

```

VHDL code for ALU Control Unit of the MIPS processor:

```

-- fpga4student.com: FPGA projects, Verilog projects, VHDL projects
-- VHDL project: VHDL code for single-cycle MIPS Processor
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
-- VHDL code for ALU Control Unit of the MIPS Processor
entity ALU_Control_VHDL is
port(
    ALU_Control: out std_logic_vector(2 downto 0);
    ALUOp : in std_logic_vector(1 downto 0);
    ALU_Funct : in std_logic_vector(2 downto 0)
);
end ALU_Control_VHDL;

architecture Behavioral of ALU_Control_VHDL is
begin
    process(ALUOp,ALU_Funct)
    begin
        case ALUOp is
        when "00" =>
            ALU_Control <= ALU_Funct(2 downto 0);
        when "01" =>
            ALU_Control <= "001";
        when "10" =>
            ALU_Control <= "100";
        when "11" =>
            ALU_Control <= "000";
        when others => ALU_Control <= "000";
        end case;
    end process;
end Behavioral;

```

VHDL code for Register File of the MIPS processor:

```

-- fpga4student.com: FPGA projects, Verilog projects, VHDL projects
-- VHDL project: VHDL code for single-cycle MIPS Processor
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
USE IEEE.numeric_std.all;
-- VHDL code for the register file of the MIPS Processor
entity register_file_VHDL is
port (
    clk,rst: in std_logic;
    reg_write_en: in std_logic;
    reg_write_dest: in std_logic_vector(2 downto 0);

```

```

reg_write_data: in std_logic_vector(15 downto 0);
reg_read_addr_1: in std_logic_vector(2 downto 0);
reg_read_data_1: out std_logic_vector(15 downto 0);
reg_read_addr_2: in std_logic_vector(2 downto 0);
reg_read_data_2: out std_logic_vector(15 downto 0)
);
end register_file_VHDL;

architecture Behavioral of register_file_VHDL is
type reg_type is array (0 to 7 ) of std_logic_vector (15 downto 0);
signal reg_array: reg_type;
begin
process(clk,rst)
begin
if(rst='1') then
reg_array(0) <= x"0001";
reg_array(1) <= x"0002";
reg_array(2) <= x"0003";
reg_array(3) <= x"0004";
reg_array(4) <= x"0005";
reg_array(5) <= x"0006";
reg_array(6) <= x"0007";
reg_array(7) <= x"0008";
elsif(rising_edge(clk)) then
if(reg_write_en='1') then
reg_array(to_integer(unsigned(reg_write_dest))) <= reg_write_data;
end if;
end if;
end process;

reg_read_data_1 <= x"0000" when reg_read_addr_1 = "000" else reg_array(to_integ
reg_read_data_2 <= x"0000" when reg_read_addr_2 = "000" else reg_array(to_integ

end Behavioral;

```

VHDL code for Control Unit of the MIPS processor:

```

-- fpga4student.com: FPGA projects, Verilog projects, VHDL projects
-- VHDL project: VHDL code for single-cycle MIPS Processor
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
-- VHDL code for Control Unit of the MIPS Processor
entity control_unit_VHDL is
port (
opcode: in std_logic_vector(2 downto 0);
reset: in std_logic;
reg_dst,mem_to_reg,alu_op: out std_logic_vector(1 downto 0);
jump,branch,mem_read,mem_write,alu_src,reg_write,sign_or_zero: out std_logic
);
end control_unit_VHDL;

architecture Behavioral of control_unit_VHDL is

begin
process(reset,opcode)

```

```
begin
  if(reset = '1') then
    reg_dst <= "00";
    mem_to_reg <= "00";
    alu_op <= "00";
    jump <= '0';
    branch <= '0';
    mem_read <= '0';
    mem_write <= '0';
    alu_src <= '0';
    reg_write <= '0';
    sign_or_zero <= '1';
  else
    case opcode is
      when "000" => -- add
        reg_dst <= "01";
        mem_to_reg <= "00";
        alu_op <= "00";
        jump <= '0';
        branch <= '0';
        mem_read <= '0';
        mem_write <= '0';
        alu_src <= '0';
        reg_write <= '1';
        sign_or_zero <= '1';
      when "001" => -- sliu
        reg_dst <= "00";
        mem_to_reg <= "00";
        alu_op <= "10";
        jump <= '0';
        branch <= '0';
        mem_read <= '0';
        mem_write <= '0';
        alu_src <= '1';
        reg_write <= '1';
        sign_or_zero <= '0';
      when "010" => -- j
        reg_dst <= "00";
        mem_to_reg <= "00";
        alu_op <= "00";
        jump <= '1';
        branch <= '0';
        mem_read <= '0';
        mem_write <= '0';
        alu_src <= '0';
        reg_write <= '0';
        sign_or_zero <= '1';
      when "011" => -- jal
        reg_dst <= "10";
        mem_to_reg <= "10";
        alu_op <= "00";
        jump <= '1';
        branch <= '0';
        mem_read <= '0';
        mem_write <= '0';
```

```
alu_src <= '0';
reg_write <= '1';
sign_or_zero <= '1';
when "100" =>-- lw
    reg_dst <= "00";
    mem_to_reg <= "01";
    alu_op <= "11";
    jump <= '0';
    branch <= '0';
    mem_read <= '1';
    mem_write <= '0';
    alu_src <= '1';
    reg_write <= '1';
    sign_or_zero <= '1';
when "101" => -- sw
    reg_dst <= "00";
    mem_to_reg <= "00";
    alu_op <= "11";
    jump <= '0';
    branch <= '0';
    mem_read <= '0';
    mem_write <= '1';
    alu_src <= '1';
    reg_write <= '0';
    sign_or_zero <= '1';
when "110" => -- beq
    reg_dst <= "00";
    mem_to_reg <= "00";
    alu_op <= "01";
    jump <= '0';
    branch <= '1';
    mem_read <= '0';
    mem_write <= '0';
    alu_src <= '0';
    reg_write <= '0';
    sign_or_zero <= '1';
when "111" =>-- addi
    reg_dst <= "00";
    mem_to_reg <= "00";
    alu_op <= "11";
    jump <= '0';
    branch <= '0';
    mem_read <= '0';
    mem_write <= '0';
    alu_src <= '1';
    reg_write <= '1';
    sign_or_zero <= '1';
when others =>
    reg_dst <= "01";
    mem_to_reg <= "00";
    alu_op <= "00";
    jump <= '0';
    branch <= '0';
    mem_read <= '0';
    mem_write <= '0';
```

```

alu_src <= '0';
reg_write <= '1';
sign_or_zero <= '1';
end case;
end if;
end process;

end Behavioral;

```

VHDL code for Instruction Memory of the MIPS processor:

```

-- fpga4student.com: FPGA projects, Verilog projects, VHDL projects
-- VHDL project: VHDL code for single-cycle MIPS Processor
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
USE IEEE.numeric_std.all;
-- VHDL code for the Instruction Memory of the MIPS Processor
entity Instruction_Memory_VHDL is
port (
  pc: in std_logic_vector(15 downto 0);
  instruction: out std_logic_vector(15 downto 0)
);
end Instruction_Memory_VHDL;

architecture Behavioral of Instruction_Memory_VHDL is
signal rom_addr: std_logic_vector(3 downto 0);
-- lw $3, 0($0) -- pc=0
-- Loop: sltiu $1, $3, 11= pc = 2
-- beq $1, $0, Skip = 4 --PCnext=PC_current+2+BranchAddr
-- add $4, $4, $3 = 6
-- addi $3, $3, 1 = 8
-- beq $0, $0, Loop--a
-- Skip c = 12 = 4 + 2 + br
type ROM_type is array (0 to 15 ) of std_logic_vector(15 downto 0);
constant rom_data: ROM_type:= (
  "1000000110000000",
  "0010110010001011",
  "1100010000000011",
  "0001000111000000",
  "1110110110000001",
  "1100000001111011",
  "0000000000000000",
  "0000000000000000",
  "0000000000000000",
  "0000000000000000",
  "0000000000000000",
  "0000000000000000",
  "0000000000000000",
  "0000000000000000",
  "0000000000000000",
  "0000000000000000"
);
begin

rom_addr <= pc(4 downto 1);
instruction <= rom_data(to_integer(unsigned(rom_addr))) when pc < x"0020" else

```

```
end Behavioral;
```

VHDL code for the MIPS Processor:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.std_logic_signed.all;
-- fpga4student.com: FPGA projects, Verilog projects, VHDL projects
-- VHDL project: VHDL code for single-cycle MIPS Processor
entity MIPS_VHDL is
port (
  clk,reset: in std_logic;
  pc_out, alu_result: out std_logic_vector(15 downto 0)
);
end MIPS_VHDL;

architecture Behavioral of MIPS_VHDL is
  signal pc_current: std_logic_vector(15 downto 0);
  signal pc_next,pc2: std_logic_vector(15 downto 0);
  signal instr: std_logic_vector(15 downto 0);
  signal reg_dst,mem_to_reg,alu_op: std_logic_vector(1 downto 0);
  signal jump,branch,mem_read,mem_write,alu_src,reg_write: std_logic;
  signal reg_write_dest: std_logic_vector(2 downto 0);
  signal reg_write_data: std_logic_vector(15 downto 0);
  signal reg_read_addr_1: std_logic_vector(2 downto 0);
  signal reg_read_data_1: std_logic_vector(15 downto 0);
  signal reg_read_addr_2: std_logic_vector(2 downto 0);
  signal reg_read_data_2: std_logic_vector(15 downto 0);
  signal sign_ext_im,read_data2,zero_ext_im,imm_ext: std_logic_vector(15 downto 0);
  signal JRControl: std_logic;
  signal ALU_Control: std_logic_vector(2 downto 0);
  signal ALU_out: std_logic_vector(15 downto 0);
  signal zero_flag: std_logic;
  signal im_shift_1, PC_j, PC_beq, PC_4beq,PC_4beqj,PC_jr: std_logic_vector(15 downto 0);
  signal beq_control: std_logic;
  signal jump_shift_1: std_logic_vector(14 downto 0);
  signal mem_read_data: std_logic_vector(15 downto 0);
  signal no_sign_ext: std_logic_vector(15 downto 0);
  signal sign_or_zero: std_logic;
  signal tmp1: std_logic_vector(8 downto 0);
begin
  -- PC of the MIPS Processor in VHDL
  process(clk,reset)
  begin
    if(reset='1') then
      pc_current <= x"0000";
    elsif(rising_edge(clk)) then
      pc_current <= pc_next;
    end if;
  end process;
  -- PC + 2
  pc2 <= pc_current + x"0002";
  -- instruction memory of the MIPS Processor in VHDL
  Instruction_Memory: entity work.Instruction_Memory_VHDL
```



```

    port map
    (
        pc=> pc_current,
        instruction => instr
    );
-- jump shift left 1
jump_shift_1 <= instr(13 downto 0) & '0';
-- control unit of the MIPS Processor in VHDL
control: entity work.control_unit_VHDL
    port map
    (reset => reset,
        opcode => instr(15 downto 13),
        reg_dst => reg_dst,
        mem_to_reg => mem_to_reg,
        alu_op => alu_op,
        jump => jump,
        branch => branch,
        mem_read => mem_read,
        mem_write => mem_write,
        alu_src => alu_src,
        reg_write => reg_write,
        sign_or_zero => sign_or_zero
    );
-- multiplexer regdest
reg_write_dest <= "111" when reg_dst= "10" else
    instr(6 downto 4) when reg_dst= "01" else
    instr(9 downto 7);
-- register file instantiation of the MIPS Processor in VHDL
reg_read_addr_1 <= instr(12 downto 10);
reg_read_addr_2 <= instr(9 downto 7);
register_file: entity work.register_file_VHDL
    port map
    (
        clk => clk,
        rst => reset,
        reg_write_en => reg_write,
        reg_write_dest => reg_write_dest,
        reg_write_data => reg_write_data,
        reg_read_addr_1 => reg_read_addr_1,
        reg_read_data_1 => reg_read_data_1,
        reg_read_addr_2 => reg_read_addr_2,
        reg_read_data_2 => reg_read_data_2
    );
-- sign extend
tmp1 <= (others => instr(6));
sign_ext_im <= tmp1 & instr(6 downto 0);
zero_ext_im <= "00000000" & instr(6 downto 0);
imm_ext <= sign_ext_im when sign_or_zero='1' else zero_ext_im;
-- JR control unit of the MIPS Processor in VHDL
JRControl <= '1' when ((alu_op="00") and (instr(3 downto 0)="1000")) else '0';
-- ALU control unit of the MIPS Processor in VHDL
ALUControl: entity work.ALU_Control_VHDL port map
    (
        ALUOp => alu_op,
        ALU_Funct => instr(2 downto 0),

```

```

    ALU_Control => ALU_Control
  );
-- multiplexer alu_src
  read_data2 <= imm_ext when alu_src='1' else reg_read_data_2;
-- ALU unit of the MIPS Processor in VHDL
alu: entity work.ALU_VHDL port map
(
  a => reg_read_data_1,
  b => read_data2,
  alu_control => ALU_Control,
  alu_result => ALU_out,
  zero => zero_flag
);
-- immediate shift 1
  im_shift_1 <= imm_ext(14 downto 0) & '0';
  no_sign_ext <= (not im_shift_1) + x"0001";
-- PC beq add
  PC_beq <= (pc2 - no_sign_ext) when im_shift_1(15) = '1' else (pc2 +im_shift_1);
-- beq control
  beq_control <= branch and zero_flag;
-- PC_beq
  PC_4beq <= PC_beq when beq_control='1' else pc2;
-- PC_j
  PC_j <= pc2(15) & jump_shift_1;
-- PC_4beqj
  PC_4beqj <= PC_j when jump = '1' else PC_4beq;
-- PC_jr
  PC_jr <= reg_read_data_1;
-- PC_next
  pc_next <= PC_jr when (JRControl='1') else PC_4beqj;
-- data memory of the MIPS Processor in VHDL
data_memory: entity work.Data_Memory_VHDL port map
(
  clk => clk,
  mem_access_addr => ALU_out,
  mem_write_data => reg_read_data_2,
  mem_write_en => mem_write,
  mem_read => mem_read,
  mem_read_data => mem_read_data
);
-- write back of the MIPS Processor in VHDL
  reg_write_data <= pc2 when (mem_to_reg = "10") else
    mem_read_data when (mem_to_reg = "01") else ALU_out;
-- output
  pc_out <= pc_current;
  alu_result <= ALU_out;

end Behavioral;

```

VHDL testbench for the MIPS processor:

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
-- fpga4student.com: FPGA projects, Verilog projects, VHDL projects
-- VHDL project: VHDL code for single-cycle MIPS Processor


```

```
-- VHDL testbench code for single-cycle MIPS Processor
ENTITY tb_MIPS_VHDL IS
END tb_MIPS_VHDL;

ARCHITECTURE behavior OF tb_MIPS_VHDL IS
    -- Component Declaration for the single-cycle MIPS Processor in VHDL
    COMPONENT MIPS_VHDL
    PORT(
        clk : IN  std_logic;
        reset : IN  std_logic;
        pc_out : OUT  std_logic_vector(15 downto 0);
        alu_result : OUT  std_logic_vector(15 downto 0)
    );
    END COMPONENT;
--Inputs
signal clk : std_logic := '0';
signal reset : std_logic := '0';
--Outputs
signal pc_out : std_logic_vector(15 downto 0);
signal alu_result : std_logic_vector(15 downto 0);
-- Clock period definitions
constant clk_period : time := 10 ns;
BEGIN
    -- Instantiate the for the single-cycle MIPS Processor in VHDL
    uut: MIPS_VHDL PORT MAP (
        clk => clk,
        reset => reset,
        pc_out => pc_out,
        alu_result => alu_result
    );

    -- Clock process definitions
    clk_process :process
    begin
        clk <= '0';
        wait for clk_period/2;
        clk <= '1';
        wait for clk_period/2;
    end process;
    -- Stimulus process
    stim_proc: process
    begin
        reset <= '1';
        wait for clk_period*10;
        reset <= '0';
        -- insert stimulus here
        wait;
    end process;
END;
```

 Simulation Waveform for the MIPS processor in VHDL:



You can change the instructions in the instruction memory and run the simulation for many different combinations of the instructions.

[Verilog code for Pipelined MIPS Processor](#)

[Verilog code for RISC Processor](#)

[Verilog code for single-cycle MIPS Processor](#)

Recommended VHDL projects:

1. [What is an FPGA? How VHDL works on FPGA](#)
2. [VHDL code for FIFO memory](#)
3. [VHDL code for FIR Filter](#)
4. [VHDL code for 8-bit Microcontroller](#)
5. [VHDL code for Matrix Multiplication](#)
6. [VHDL code for Switch Tail Ring Counter](#)
7. [VHDL code for digital alarm clock on FPGA](#)
8. [VHDL code for 8-bit Comparator](#)
9. [How to load a text file into FPGA using VHDL](#)
10. [VHDL code for D Flip Flop](#)
11. [VHDL code for Full Adder](#)
12. [PWM Generator in VHDL with Variable Duty Cycle](#)
13. [VHDL code for ALU](#)
14. [VHDL code for counters with testbench](#)
15. [VHDL code for 16-bit ALU](#)
16. [Shifter Design in VHDL](#)
17. [Non-linear Lookup Table Implementation in VHDL](#)
18. [Cryptographic Coprocessor Design in VHDL](#)
19. [Verilog vs VHDL: Explain by Examples](#)
20. [VHDL Code for Clock Divider on FPGA](#)
21. [How to generate a clock enable signal instead of creating another clock domain](#)
22. [VHDL code for debouncing buttons on FPGA](#)
23. [VHDL code for Traffic light controller](#)
24. [VHDL code for a simple 2-bit comparator](#)
25. [VHDL code for a single-port RAM](#)
26. [VHDL code for Car Parking System using FSM](#)
27. [VHDL coding vs Software Programming](#)
28. [VHDL code for MIPS Processor](#)
29. [VHDL code for Moore FSM Sequence Detector](#)
30. [VHDL code for Seven-Segment Display on Basys 3 FPGA](#)

21
SHARES



2 comments:



Unknown May 15, 2020 at 1:04 PM

do you implement 32 bit MIPS with SIMD

[Reply](#)



Unknown May 15, 2020 at 1:50 PM

dear i run the whole project, but can't see the same output which you attach at the end. can you share with me further details?? Thanks

[Reply](#)

Enter your comment...



Comment as: prof.hosam010 ▼

[Sign out](#)

[Publish](#)

[Preview](#)

☐ [Notify me](#)



[Home](#)



[View web version](#)



BECOME A PATRON

Join 18,000+ Followers



Subscribe to More Upcoming FPGA/Verilog/VHDL Projects

Email your email address...

Submit



[Privacy Policy](#) | [Disclaimer](#) | [Sitemap](#) | [Contact](#) | [Advertise Here](#)
Copyright © 2016-2020 FPGA4student.com All Rights Reserved.
